 


Circuits

CMSC250


Announcements / Reminders / Schedule

- Recording of Sunday's review session is [up](#).
- Homework 4 solutions are also [up](#).
 - Consult them if you have questions about combinatorial proof structure, or other questions!
- Remember:
 - No hw this week
 - No quiz this week
 - But next week there **will** be both! 😊😐😞
- Today & Thursday: circuits!



Announcements / Reminders / Schedule

- Expectation of grading:
 - Homework 4 grading comes first, by Monday.
 - Midterm grading will take extra time (Friday 03-12).
 - You will have a full week (through Friday 03-19, Springbreak Friday) to submit regrade requests on Gradescope.
- Midterm solutions posted as soon as Thursday 08:01 AM
 - Probably a bit later, to avoid last – minute panic of any kind.
- Logic behind solving will be covered in one of the two discussion sessions next week.

 

Circuits

- We can build circuits for addition, multiplication, division, bit shifting...
- Every logical operation we have learned (\sim, \wedge, \vee) maps straightforwardly to a tiny piece of hardware called a *logical gate*.
- These gates connect to each other to make arbitrarily complicated circuits!

From a truth table to a formula

p	q	r	output
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

From a truth table to a formula

p	q	r	output
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

- Let us focus entirely on the rows that output 1!

p	q	r	output
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Focusing on the 1st row...

p	q	r	output
0	0	0	1

- Write a simple formula that is '1' only on inputs p =0, q = 0, r = 0.

p	q	r	output
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Focusing on the 1st row...

p	q	r	output
0	0	0	1

- Write a simple formula that is '1' only on inputs p = 0, q = 0, r = 0.

$$\sim p \wedge \sim q \wedge \sim r$$

p	q	r	output
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Focusing on the 4th row...

p	q	r	output
0	1	1	1

- Same deal

p	q	r	output
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Focusing on the 4th row...

p	q	r	output
0	1	1	1

- Same deal

$$\sim p \wedge q \wedge r$$

p	q	r	output
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Focusing on the 5th row...

p	q	r	output
1	0	0	1

$$p \wedge \sim q \wedge \sim r$$

p	q	r	output
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Focusing on the 8th row...

p	q	r	output
1	1	1	1

$p \wedge q \wedge r$

How do we combine those simple formulae?

$$\sim p \wedge \sim q \wedge \sim r$$

$$\sim p \wedge q \wedge r$$

$$p \wedge \sim q \wedge \sim r$$

$$p \wedge q \wedge r$$

How do we combine those simple formulae?

$$(\sim p \wedge \sim q \wedge \sim r) \vee$$

$$(\sim p \wedge q \wedge r) \vee$$

$$(p \wedge \sim q \wedge \sim r) \vee$$

$$(p \wedge q \wedge r)$$

p	q	r	output
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

- Outputs 1 if and only if the truth table outputs 1!

How do we combine those simple formulae?

$$(\sim p \wedge \sim q \wedge \sim r) \vee$$

$$(\sim p \wedge q \wedge r) \vee$$

$$(p \wedge \sim q \wedge \sim r) \vee$$


$$(p \wedge q \wedge r)$$

p	q	r	output
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

- Outputs 1 if and only if the truth table outputs 1!
- **We want to do this in hardware!**


Logical gates

 - The smallest pieces of hardware that we will examine are called ***logical gates***.
- Every gate that we encounter will take **bits** as inputs and will emit one **bit** as output.



- Those gates can connect to each other in various different ways in order to create more complex circuits

Our first gate

 

<i>A</i>	<i>out</i>
0	1
1	0

- This gate is known as the **inverter**.
- It corresponds **exactly** to the negation operation in propositional logic!
 - Where 1, set True.
 - Where 0, set False

Our second gate



p	q	r
0	0	0
0	1	0
1	0	0
1	1	1

- Corresponds to:

Conjunction


Disjunction

Our second gate (AND gate)




p	q	r
0	0	0
0	1	0
1	0	0
1	1	1

- Corresponds to:

 

Our second gate (AND gate)

 

p	q	r
0	0	0
0	1	0
1	0	0
1	1	1

- Corresponds to:

Conjunction

Disjunction

Our third gate (OR gate)




p	q	r
0	0	0
0	1	1
1	0	1
1	1	1

- Corresponds to logical disjunction (OR)

 
Exercises

- Which boolean function does this circuit correspond to?



 Exercises


- Which boolean function does this circuit correspond to?



$$(p \wedge s) \vee r$$


Exercises

- And this?

 


Exercises

- And this?

 


$$(m \wedge n) \vee (\sim (k \wedge l))$$

And this?

 


And this?

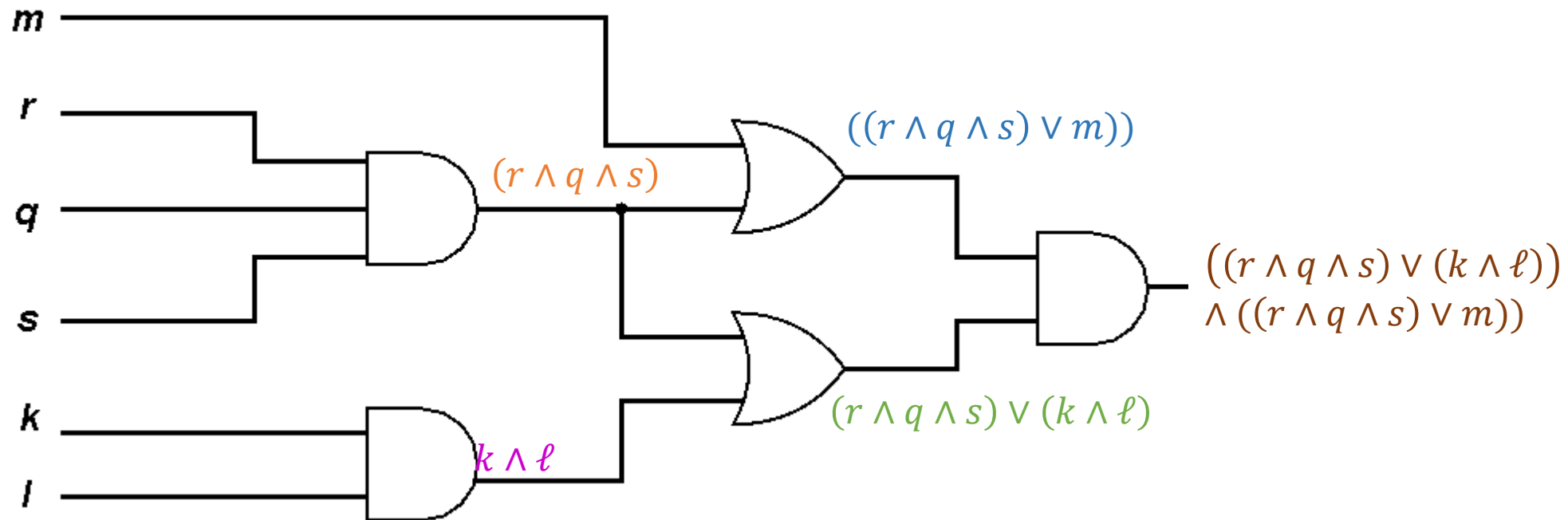

$$((r \wedge q \wedge s) \vee (k \wedge \ell)) \wedge ((r \wedge q \wedge s) \vee m)$$

And this?


Can we make this
circuit *cheaper*?

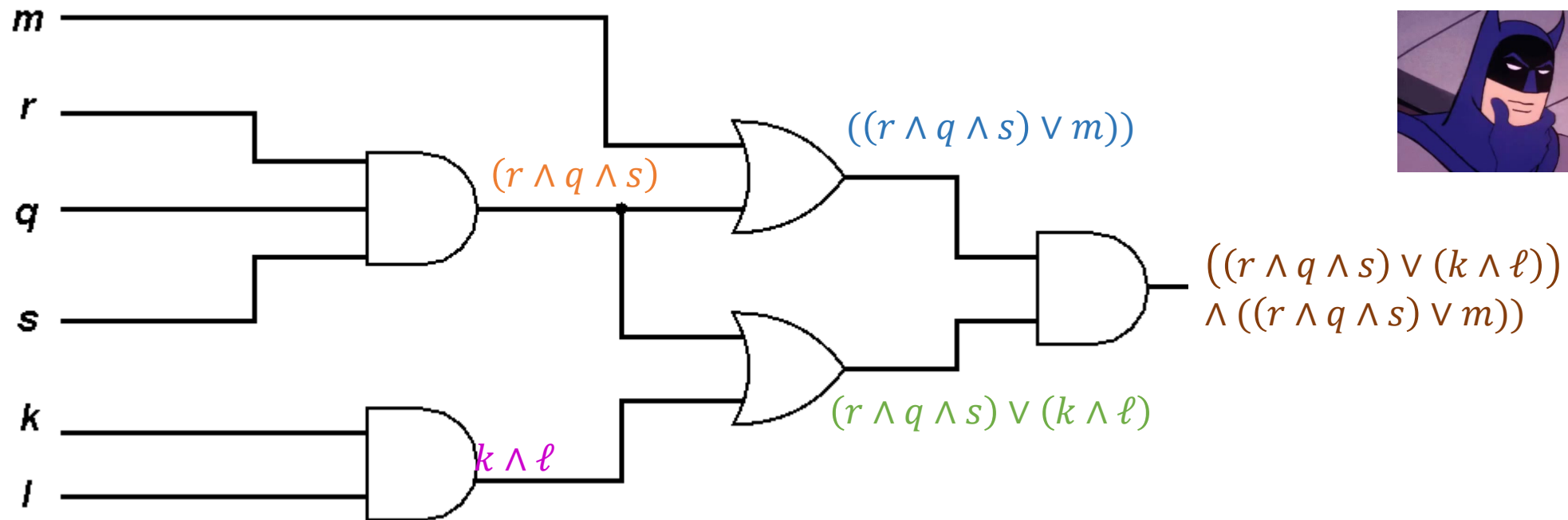


$$((r \wedge q \wedge s) \vee (k \wedge l)) \wedge ((r \wedge q \wedge s) \vee m)$$

Simplifying the circuit...
 
$$\begin{aligned} & ((r \wedge q \wedge s) \vee (k \wedge \ell)) \wedge ((r \wedge q \wedge s) \vee m) \\ \equiv & (r \wedge q \wedge s) \vee ((k \wedge \ell) \wedge m) \end{aligned}$$




New circuit: Three gates

 

Old circuit: Five gates


Exercises

 1. Which logical expression is computed by the following circuit?



Exercises

 1. Which logical expression is computed by the following circuit?
2. *Simplify* the circuit as much as possible!



Coming back to our original formula...

$$(\sim p \wedge \sim q \wedge \sim r) \vee (\sim p \wedge q \wedge r) \vee (p \wedge \sim q \wedge \sim r) \vee (p \wedge q \wedge r)$$

Coming back to our original formula...


$$(\sim p \wedge \sim q \wedge \sim r) \vee (\sim p \wedge q \wedge r) \vee (p \wedge \sim q \wedge \sim r) \vee (p \wedge q \wedge r)$$

- For each small formula we have a circuit, and we will combine with a 4-input OR gate!

Coming back to our original formula...


$$(\sim p \wedge \sim q \wedge \sim r) \vee (\sim p \wedge q \wedge r) \vee (p \wedge \sim q \wedge \sim r) \vee (p \wedge q \wedge r)$$

- For each small formula we have a circuit, and we will combine with a 4-input OR gate!

 


Circuit 1

$$(\sim p \wedge \sim q \wedge \sim r)$$

 


Circuit 2

$$(\sim p \wedge q \wedge r)$$

 


Circuit 3

$$(p \wedge \sim q \wedge \sim r)$$

 

Circuit 4

$$(p \wedge q \wedge r)$$

 

Midterm news / reminders

- Panic-free midterm!
- We will take an extra day or two to publish solutions
 - In case somebody has had an emergency / ER / hospital visit / any other emergency.
 - Monday: you will cover the midterm and have questions from today answered.
- Today: Adder circuits!
 - This concludes the logic portion!
- Next week: Set Theory

Midterm news / reminders

- Next week: Set Theory and, possibly, quantifiers (\forall , \exists) on Thursday
 - I will probably have you ensure **on your own** what \subseteq , \cap , \cup and \in mean. **Nothing more.**
 - Either textbook, or [Wikipedia](#) / [Wolfram Alpha](#) are good resources.
- Remember: SpringBreak in two weeks.
 - Next week's homework will be designed for one week, but will have a 2-week deadline through 03-22.
 - There **will** be a short quiz **next week**, which you will still have 1 week and 3 days to submit (Monday 03-22, 11:59pm, like your homework)
 - But come on man, it's a short quiz.


Building Adder Circuits

- We want to build circuits that add arbitrarily large binary numbers.
- E.g

$$\begin{array}{r} 10011001 \\ +00110011 \\ \hline 11001100 \end{array}$$

Inputs

Output

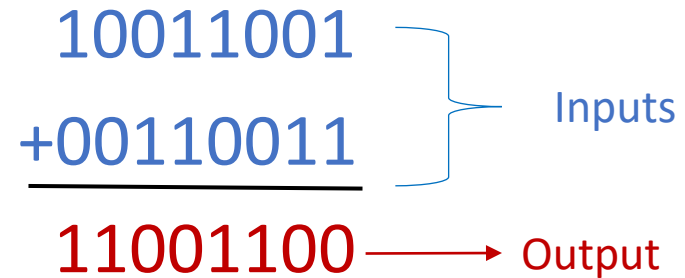

Half-Adder

- A half-adder is a circuit that adds **two bits** together!

$$\begin{array}{r} X \\ + Y \\ \hline C \ S \end{array}$$

- (Remember: C is the carry bit.)
- Let's try to build a circuit that computes both S and C !

Truth table


X	Y	S	C
0	0	?	?
0	1	?	?
1	0	?	?
1	1	?	?

Truth table

X	Y	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


Truth table

X	Y	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

Truth table

X	Y	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

XOR Gate
("Ex**cl**usive **OR**")

Making XOR cheaper


- First, let's convince ourselves that

$$(x \oplus y) \equiv (x \wedge (\sim y)) \vee ((\sim x) \wedge y) \equiv (x \vee y) \wedge (\sim(x \wedge y))$$

Making XOR cheaper

- First, let's convince ourselves that

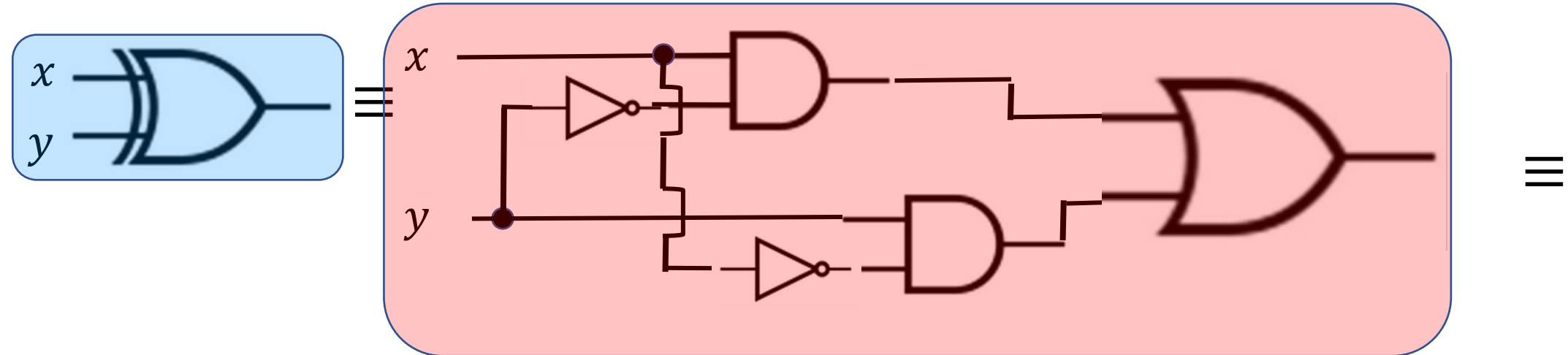
$$(x \oplus y) \equiv (x \wedge (\sim y)) \vee ((\sim x) \wedge y) \equiv (x \vee y) \wedge (\sim(x \wedge y))$$



Making XOR cheaper

- First, let's convince ourselves that

 
$$(x \oplus y) \equiv (x \wedge (\sim y)) \vee ((\sim x) \wedge y) \equiv (x \vee y) \wedge (\sim(x \wedge y))$$



Making XOR cheaper

- First, let's convince ourselves that
 
$$(x \oplus y) \equiv (x \wedge (\sim y)) \vee ((\sim x) \wedge y) \equiv (x \vee y) \wedge (\sim(x \wedge y))$$




From **five** gates to **four**!




Optimizing Half Adder

 - We can now **optimize** the Half Adder.
- We won't just use simplified XOR, but also **leverage simplified XOR** to **re-use** the **AND** gate used to compute the carry bit C !



Half Adder Abstraction

 

4 gates, instead of 6 for the previous one!



Half Adder Abstraction



Full-Adder

- Now, let's consider the complete case, where we want to build a circuit that computes the sum of two 2-digit binary numbers:

$$\begin{array}{r} P\ Q \\ + \underline{W\ X} \\ C\ S_1\ S_2 \end{array}$$

- To do this, we also need the ability to add 3 digits, because:

$$\begin{array}{r} \underline{C_1} \\ P\ Q \\ + \underline{W\ X} \\ C\ S_1\ S_2 \end{array}$$

Full-Adder

- Now, let's consider the complete case, where we want to build a circuit that computes the sum of two 2-digit binary numbers:

$$\begin{array}{r} P \ Q \\ + \underline{W \ X} \\ C \ S_1 \ S_2 \end{array}$$

- To do this, we also need the ability to add **3** digits, because:

$$\begin{array}{r} \underline{C_1} \\ P \ Q \\ + \underline{W \ X} \\ C \ S_1 \ S_2 \end{array}$$

We will call a circuit that adds 3 bits a full adder

We could do the truth table....

P Q
+ W X
C S1 S2

P	Q	W	X	C	S ₁	S ₂
0	0	0	0			
0	0	0	1			
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0			
0	1	1	1			
1	0	0	0			
1	0	0	1			
1	0	1	0			
1	0	1	1			
1	1	0	0			
1	1	0	1			
1	1	1	0			
1	1	1	1			

We could do the truth table....

P Q
+ W X
C S₁ S₂

P	Q	W	X	C	S ₁	S ₂
0	0	0	0			
0	0	0	1			
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0			
0	1	1	1			
1	0	0	0			
1	0	0	1			
1	0	1	0			
1	0	1	1			
1	1	0	0			
1	1	0	1			
1	1	1	0			
1	1	1	1			

But it's time
consuming and we
are all busy people


Constructing a Full-Adder in another way

- We need to build a circuit that computes the sum of 3 digits, e.g $P + Q + R$


- **Step 1:** Compute
$$\begin{array}{r} P \\ + Q \\ \hline C_1 S_1 \end{array}$$
 with a **half-adder**:




Constructing a Full Adder

 

 - Step 2: Compute $\begin{array}{r} +_R \\ C_2S \end{array}$ with another half-adder:




Constructing a full-adder

 


- **Step 3:** Combine C_1 and C_2 with an OR gate to yield the final carry bit C .

Constructing a full-adder

 

- Step 3: Combine C_1 and C_2 with an OR gate to yield the final carry bit C .
- Why did we choose an OR gate to combine the “intermediate” carries C_1 and C_2 ?

Constructing a full-adder

 


- **Step 3:** Combine C_1 and C_2 with an OR gate to yield the final carry bit C .

**Abstraction
time!**

Full Adder Black Box

- 3 inputs, 2 outputs

 


2-bit adder

- However, **we still have not solved our original problem**, which is to construct a circuit that adds 2-bit numbers!


$$\begin{array}{r} P\ Q \\ +\ \underline{W\ X} \\ C\ S_1\ S_2 \end{array}$$

 - So, we need a circuit that takes 4 inputs and emits 3 outputs:




Constructing a 2-bit adder

 - Step 1: Take care of the right-most column with a half-adder:



Constructing a 2-bit adder

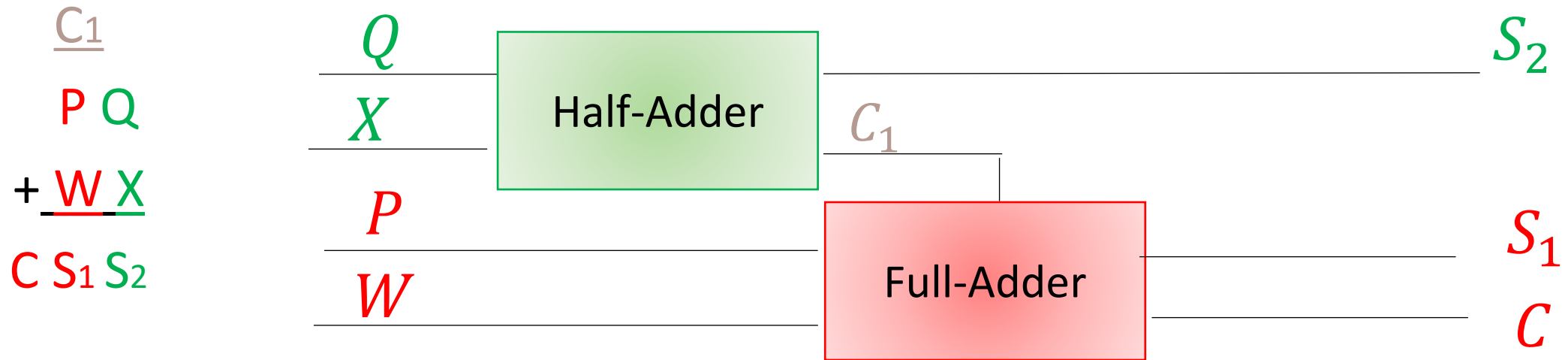
- Step 1: Take care of the **right-most column** with a **half-adder**:



- Step 2 (and final): Connect **Half-Adder** and new inputs to **Full-adder** appropriately to produce final circuit.


Constructing a 2-bit adder

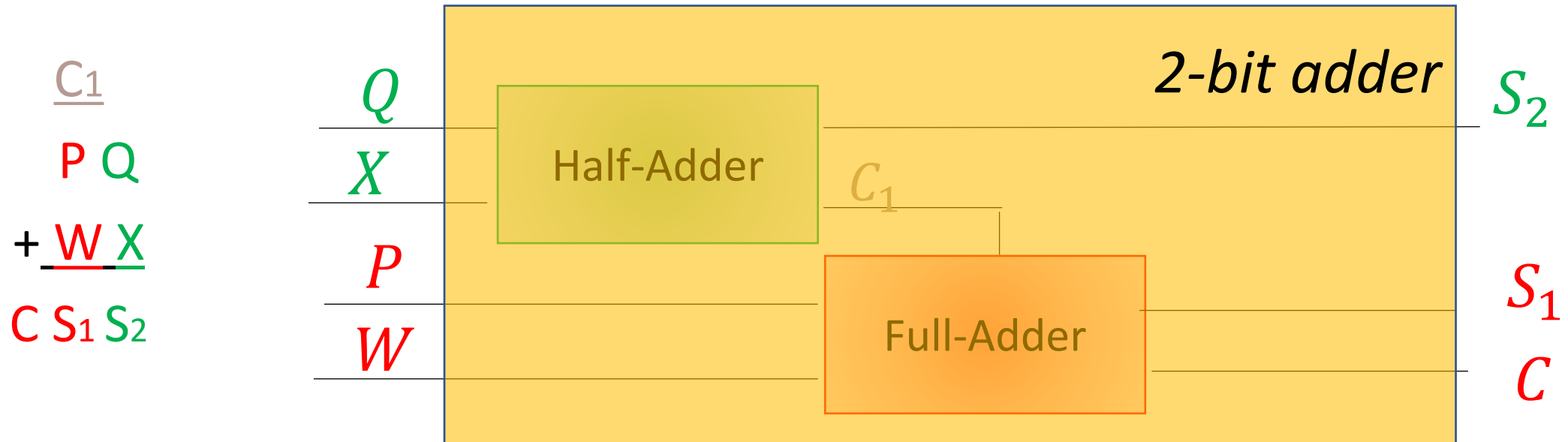- Step 1: Take care of the **right-most column** with a **half-adder**:




- Step 2 (and final): Connect **Half-Adder** and new inputs to **Full-adder** appropriately to produce **final circuit**.


Constructing a 3-bit adder (messy)

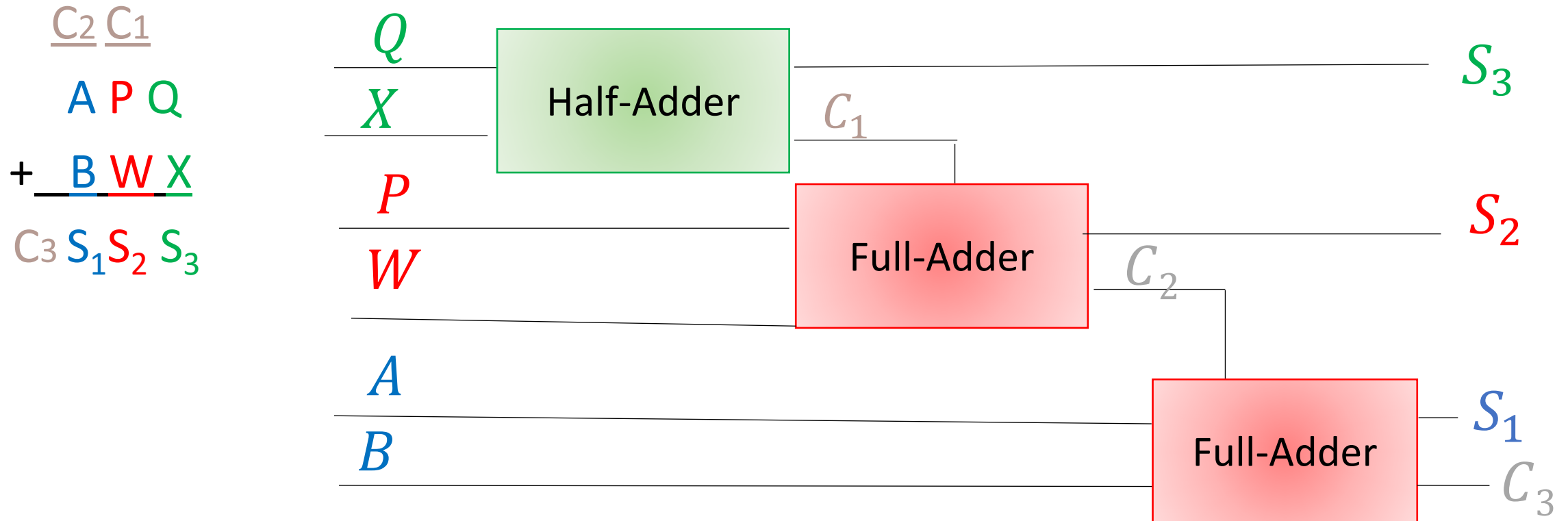


Constructing a 3-bit adder (neat)

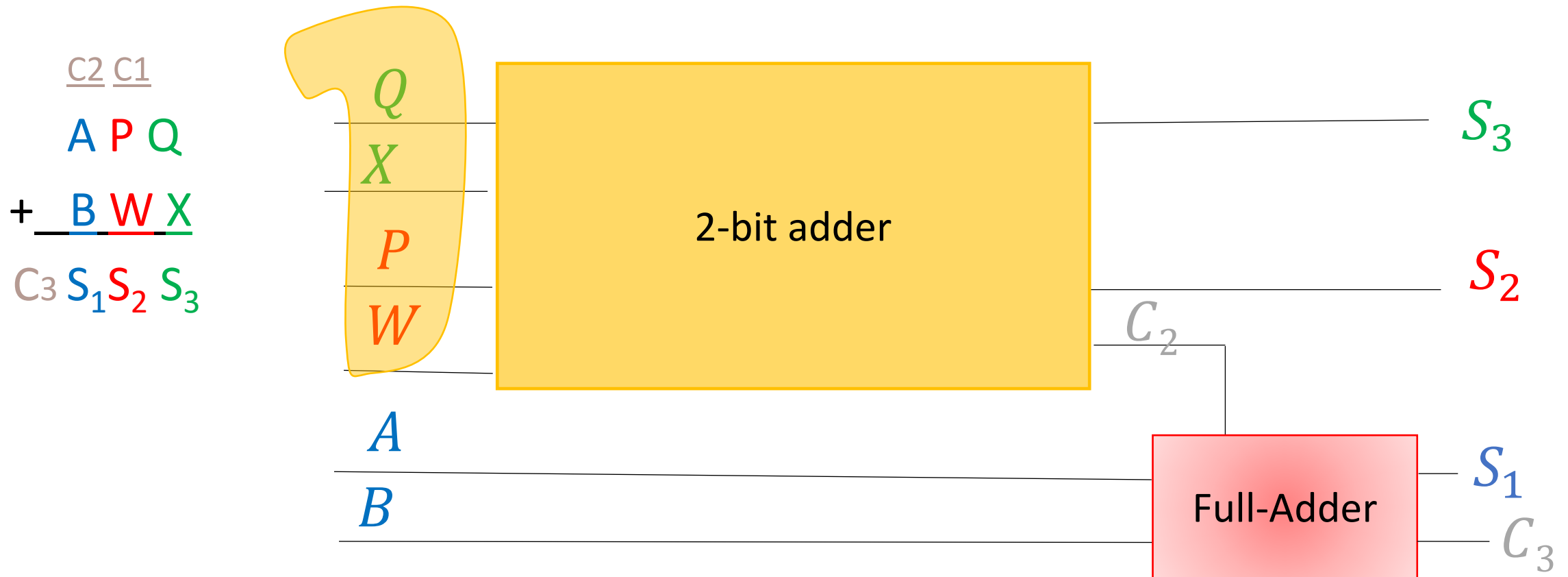

Constructing an n-bit adder (messy)

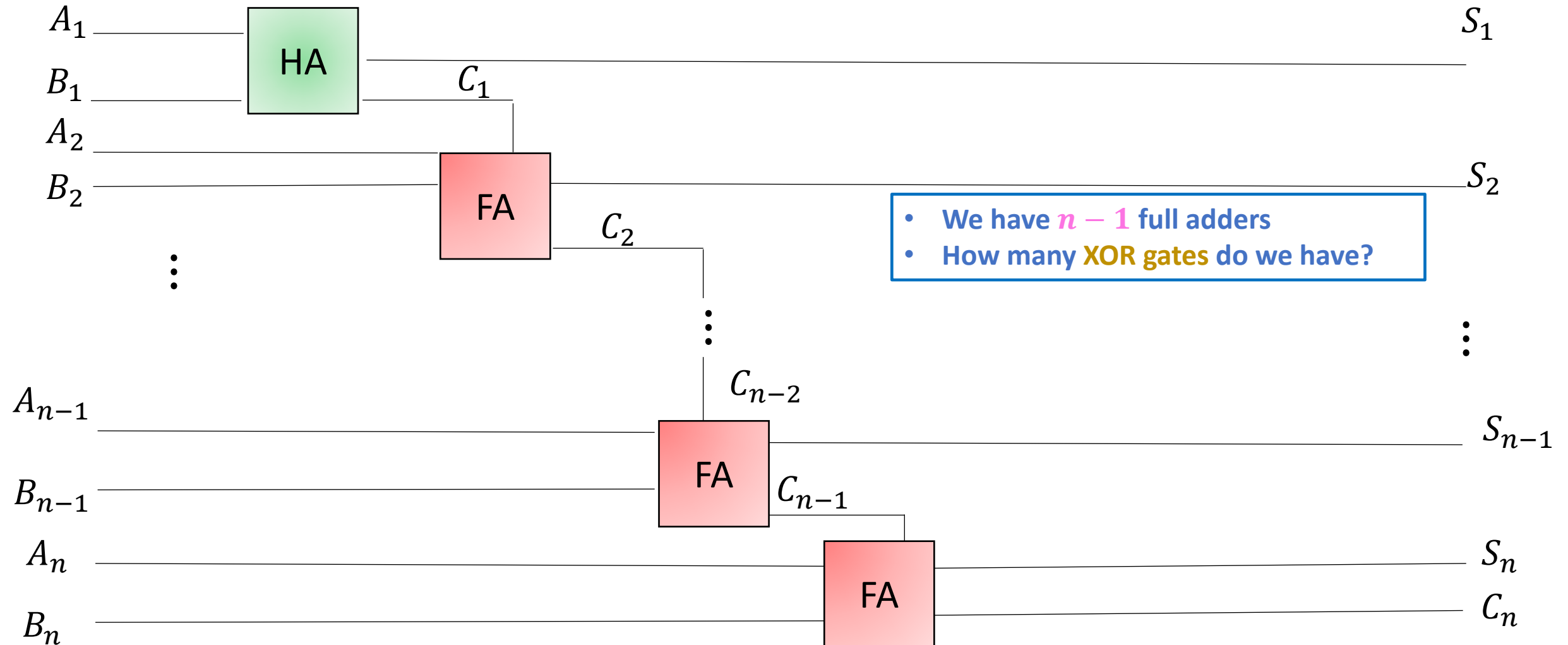


Constructing an n-bit adder (neat)

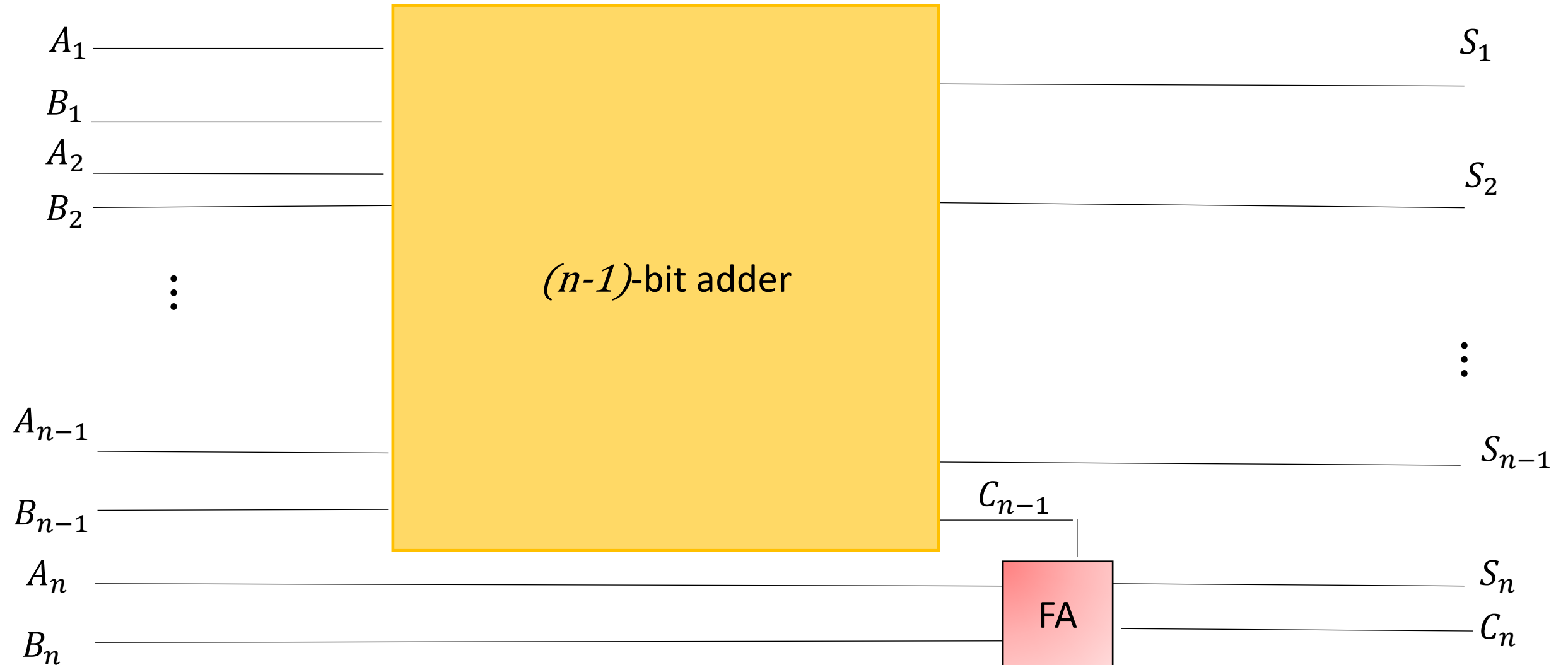

Fun exercise

- Input: number in **binary** (B_0, B_1)
- Output (in U_0, U_1, U_2): ???

B_1	B_0	U_2	U_1	U_0
0	0	0	0	0
0	1	0	0	1
1	0	0	1	1
1	1	1	1	1

 


Fun exercise

- Input: number in **binary** (B_0, B_1)
- Output (in U_0, U_1, U_2): **Binary to Unary**




B_1	B_0	U_2	U_1	U_0
0	0	0	0	0
0	1	0	0	1
1	0	0	1	1
1	1	1	1	1

 

First micro-circuit

B_1	B_0	U_2	U_1	U_0
0	0	0	0	0
0	1	0	0	1
1	0	0	1	1
1	1	1	1	1

$$U_2 = B_1 \wedge B_0$$

 

Second micro-circuit

B_1	B_0	U_2	U_1	U_0
0	0	0	0	0
0	1	0	0	1
1	0	0	1	1
1	1	1	1	1

$$U_1 = (B_1 \wedge \sim B_0) \vee (B_1 \wedge B_0)$$

Second micro-circuit

B_1	B_0	U_2	U_1	U_0
0	0	0	0	0
0	1	0	0	1
1	0	0	1	1
1	1	1	1	1

$$U_1 = (B_1 \wedge \sim B_0) \vee (B_1 \wedge B_0) = \mathbf{B_1}$$

(from distributive law of conjunction over disjunction!)

$$B_1 \longrightarrow U_1$$

Third micro-circuit


B_1	B_0	U_2	U_1	U_0
0	0	0	0	0
0	1	0	0	1
1	0	0	1	1
1	1	1	1	1

$$U_0 = (\sim B_1 \wedge B_0) \vee (B_1 \wedge \sim B_0) \vee (B_1 \wedge B_0)$$

Third micro-circuit


B_1	B_0	U_2	U_1	U_0
0	0	0	0	0
0	1	0	0	1
1	0	0	1	1
1	1	1	1	1
 
$$U_0 = (\sim B_1 \wedge B_0) \vee (B_1 \wedge \sim B_0) \vee (B_1 \wedge B_0) = (\sim B_1 \wedge B_0) \vee B_1 = (\sim B_1 \vee B_1) \wedge (B_0 \vee B_1) = B_0 \vee B_1$$



Final circuit

B_1	B_0	U_2	U_1	U_0
0	0	0	0	0
0	1	0	0	1
1	0	0	1	1
1	1	1	1	1

 

Other numeric functions

- Addition (have done)
- Multiplication
- Division
- Primality test (test whether a number is prime)
- There are circuits for all of these!
 - Computers actually work this way at the base level: they consist of gates.